

OSNOVE ELEKTROTEHNIKE

MASOVNE


$$p(t) = u(t) \cdot i(t)$$

$$\dot{S} = \dot{U} \cdot \dot{I}^* = U \cdot I \cdot [2u - 2i] = U \cdot I / \varphi$$

$$\dot{z} = \frac{\dot{U}}{\dot{I}} = \frac{U}{I} \quad \text{L} u - \text{L} i = \frac{U}{I} \varphi$$

$$\dot{S} = P + jQ$$

→ SREDNJA SNAGA = RADNA SNAGA

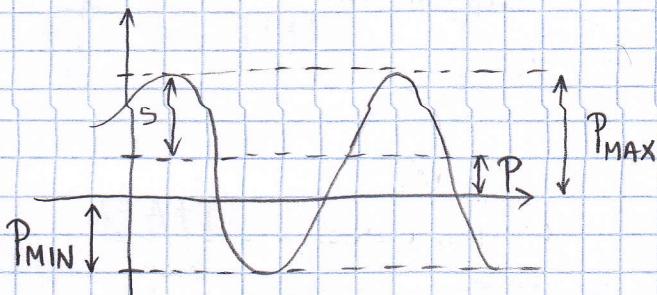

2) Na nekoj impedanciji \dot{z} je $P_{\text{MAX}} = 900 \text{ VA}$, $P_{\text{MIN}} = 100 \text{ VA}$, a $U = 50 \text{ V}$. $\dot{z} = ?$

$$P = \frac{P_{\text{MAX}} + P_{\text{MIN}}}{2} = 400 \text{ W}$$

$$S = P_{\text{MAX}} - P = 500 \text{ VA}$$

$$Q = \sqrt{S^2 - P^2} = 300 \text{ VAr}$$

$$\cos \varphi = 0,8 \rightarrow \pm 36,87^\circ$$

$$\cos \varphi = \frac{P}{S} = 0,8 \rightarrow \varphi = 36,87^\circ \quad \text{NE} \quad \rightarrow \varphi = -36,87^\circ$$

$$S = U \cdot I$$


$$I = \frac{S}{U} = 10 \text{ A}$$

$$z = \frac{U}{I} = 5 \Omega$$

$$z = 5 \angle -36,87^\circ = 4 - j3 \Omega$$

$$P = I^2 R = I^2 Z \cdot \cos \varphi = \frac{U^2}{Z} \cos \varphi = \frac{U^2}{R} \rightarrow \text{pažiti kada se koja koristi!}$$

Zad.)

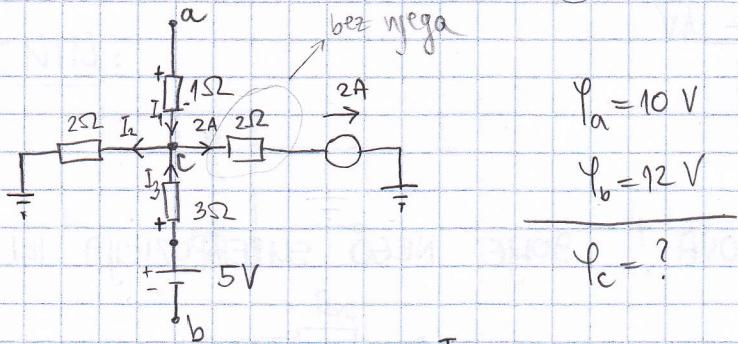

$$I_1 + I_3 = I_2 + 2$$

$$\frac{\varphi_a - \varphi_c}{1} + \frac{\varphi_b + 5 - \varphi_c}{3} = \frac{\varphi_c}{2} + 2$$

: GRUPIRANJEM ∇

! POTENCIJALI ČVOROVA $\longrightarrow \varphi_c \left[\frac{1}{1} + \frac{1}{3} + \frac{1}{2} \right] - \varphi_a \cdot \frac{1}{1} - \varphi_b \cdot \frac{1}{3} = \frac{5}{3} - 2$
 ↓
 SJETI SE !!

VODljIVOSTI U


struje

odlazi iz C

OKOLNOJ GRANI, ALI BEZ OTPORA KOJI

U SVOJOJ GRANI IMA STRUJNI IzVOR
 → želimo doći do struja (napon · otpor), a u
 toj grani već imamo struju!

Zad.)

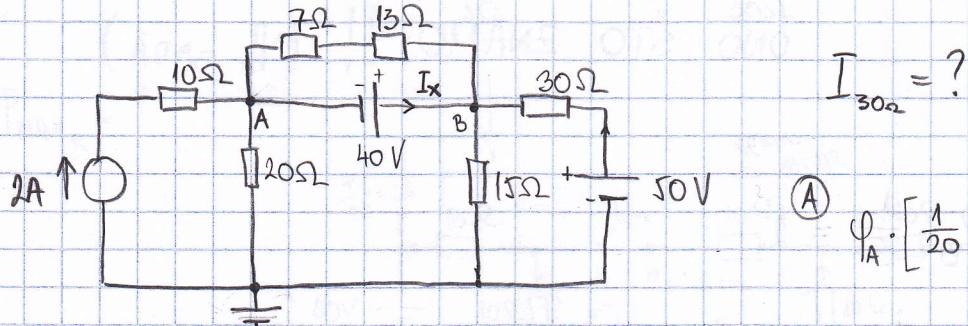

$$I_{30\Omega} = ?$$

$$\textcircled{A} \quad \varphi_A \cdot \left[\frac{1}{20} + \frac{1}{7+13} + \frac{1}{0} \right] - \varphi_B \cdot \left(\frac{1}{0} + \frac{1}{20} \right) =$$


$$= 2 - \frac{50}{20} - I_x$$

grana sa -15V

$$\textcircled{B} \quad \varphi_B \left[\frac{1}{15} + \frac{1}{30} + \frac{1}{20} \right] - \varphi_A \cdot \left(\frac{1}{7+13} \right) = \frac{50}{30} + I_x$$

$$\varphi_B = \varphi_A + 40$$

Pr.) !! NE U POT. ČV. !

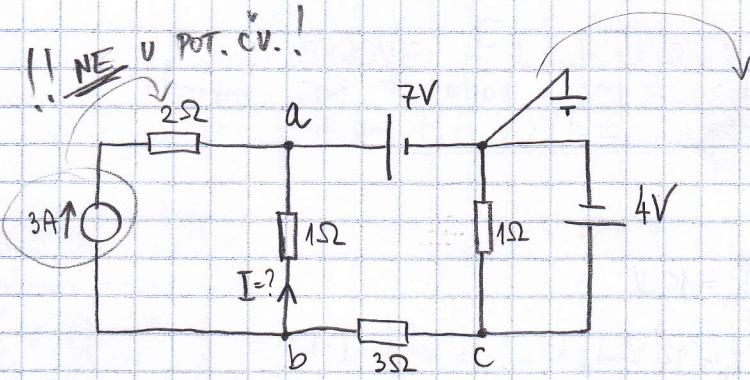


PRIKLDNO ODABRATI UZEMLJENJE!

GLEDATI POTENCIJALE ČVOROVA! BOYE NEGOT SUPERPOZICIJA ILI NESTO!

$$\begin{aligned}\varphi_a &= 7V \\ \varphi_c &= 4V\end{aligned} \quad \left. \begin{array}{l} \text{nakon što smo uzeli} \\ \text{jili!} \end{array} \right\}$$

$$\varphi_b \left(\frac{1}{1} + \frac{1}{3} \right) - \varphi_a \frac{1}{1} - \varphi_c \frac{1}{3} = -3$$

Pr. 2)

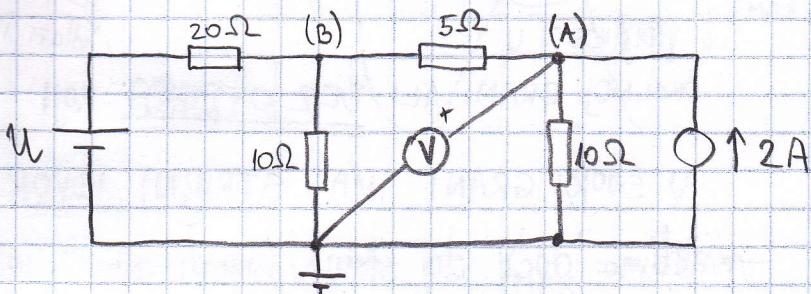

$$\frac{U_V = 10V}{U = ?}$$

PONEKAD ZAPISATI JEDNADŽBU I ZA
ONO ŠTO ZNAMO !! (φ_A SADA)

$$\varphi_A = 10V$$

$$10 \cdot \left(\frac{1}{10} + \frac{1}{5} \right) - \varphi_B \cdot \frac{1}{5} = 2$$

⋮


$$\varphi_B = 5V$$

$$5 \left(\frac{1}{20} + \frac{1}{10} + \frac{1}{5} \right) - 10 \cdot \frac{1}{5} = -\frac{U}{20}$$


$$U = 0V$$

MILLMAN → ISTO KAO POTENCIJALI ČVOROVA.

THEVENIN:

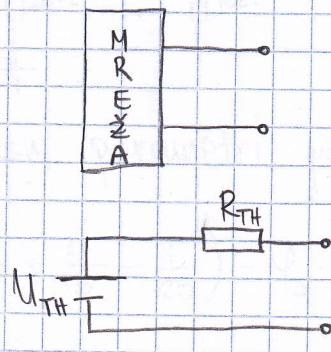


NORTON:

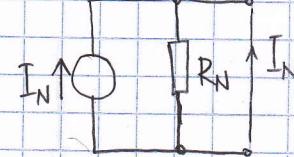


$$R_{TH} = R_N$$

$$U_{TH} = R_N \cdot I_N$$


P_r)

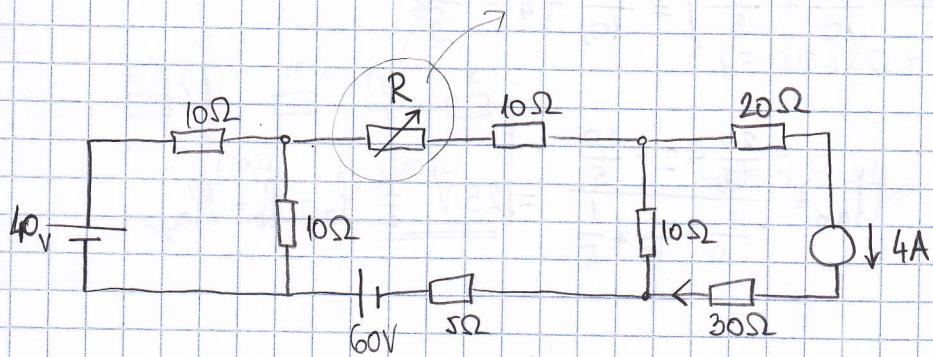

$$P_{MAX,R} = ?$$

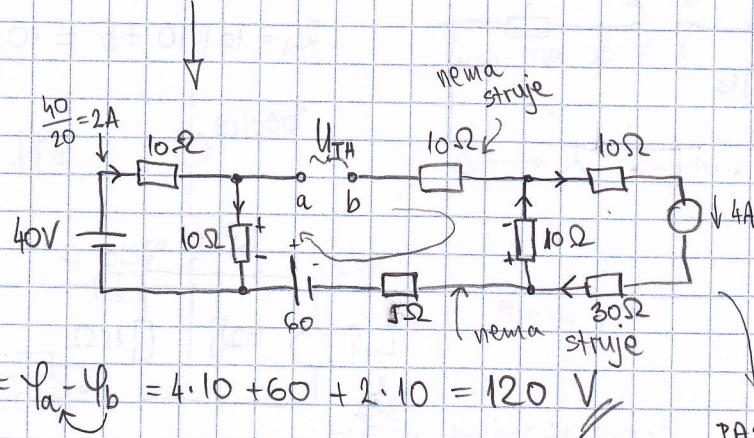

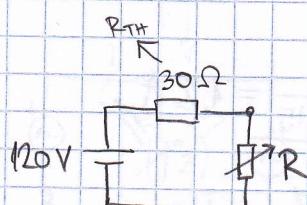NEMOJ PRENOSITI INFORMACIJE!
PASIVNA MREŽA (za R_{TH}):



P_{MAX} → kada $R = R_{TH}$ bude jednak vnutarnjem R_i

$$R_i = R_{TH} \rightarrow R = R_{TH} = 30 \Omega \rightarrow P_{MAX}$$


$$R_{ab} = R_T = 10 \parallel 10 + 5 + 10 + 10 =$$

$$R_{TH} = 30 \Omega$$


$$R_{TH} = 30 \Omega$$

$$I = 2 \text{ A} \rightarrow P_{\text{MAX}} = I^2 \cdot R = 120 \text{ W}$$

P.2.)

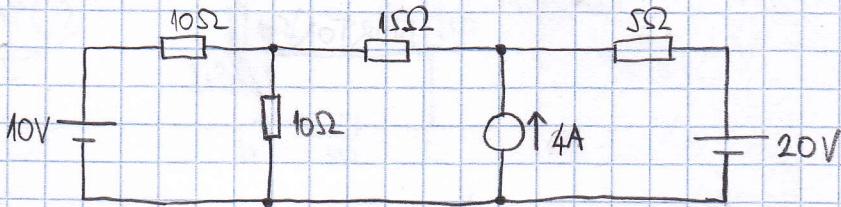


$$I_{15\Omega} = ?$$

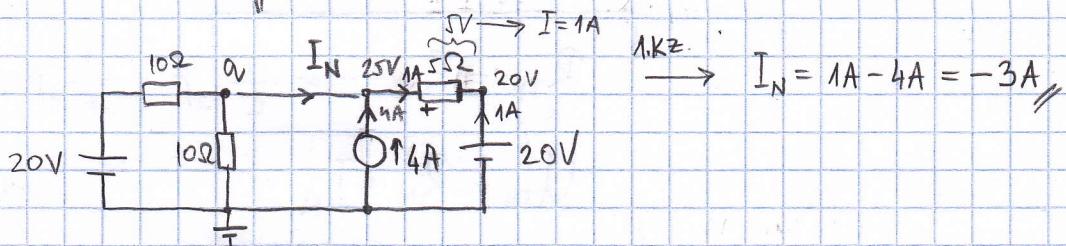


$$\varphi_a \left(\frac{1}{10} + \frac{1}{10} + \frac{1}{5} \right) = \frac{20}{10} + 4 + \frac{20}{5}$$

MILLMAN:
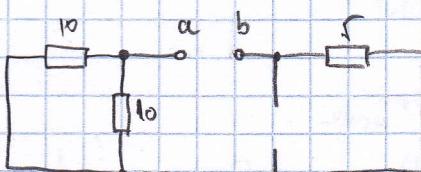
$$U_{ab} = \frac{\frac{20}{10} + 2 + \frac{20}{5}}{\frac{1}{10} + \frac{1}{10} + \frac{1}{5}} = 25 \text{ V} = \varphi_a - \varphi_b = \varphi_a$$


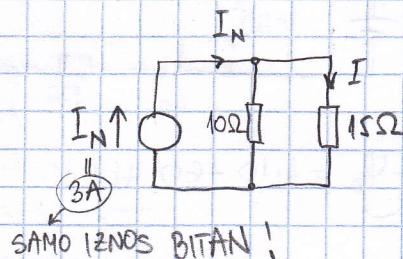
$$R_N = 10 \parallel 10 + 5 = 10 \Omega$$




SAMO IZNOŠ BITAN!

$$I = I_N \cdot \frac{10}{10+15} = 1,2 \text{ A}$$

strujno dijelilo

Pr.3)

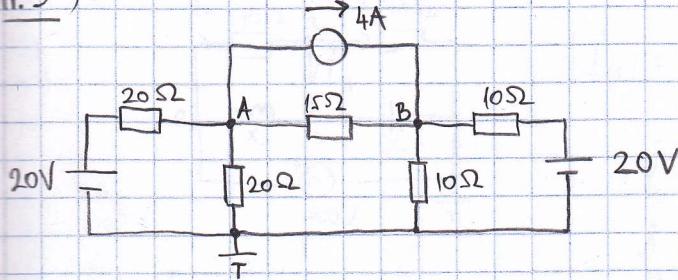


→ nadomjesni parametri po Theveninu, U_{ab} , $R_{ab} = ?$

$$\varphi_A \left(\frac{1}{20} + \frac{1}{15} + \frac{1}{20} \right) - \varphi_B \cdot \frac{1}{15} = \frac{20}{20} - 4$$

$$\varphi_B \left(\frac{1}{10} + \frac{1}{10} + \frac{1}{15} \right) - \varphi_A \cdot \frac{1}{15} = \frac{20}{10} + 4$$


$$U_{ab} = \varphi_A - \varphi_B$$

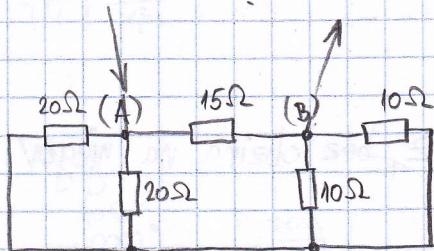

$$R_{ab} = (20 \parallel 20 + 10 \parallel 10) \parallel 15$$


$$R_{ab} = 7,5 \Omega$$

Pr.4.)

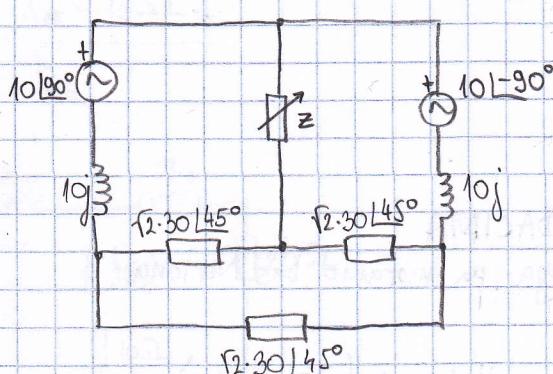


$$P_{MAX} \text{ na } Z = ?$$

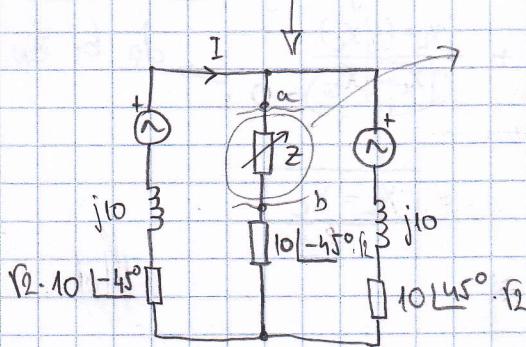$\Delta \rightarrow \lambda$ za iste 3x MANJI otpori




$$I = \frac{10 \angle 90^\circ - 10 \angle -90^\circ}{10j + 10 \angle -45^\circ + 10 \angle 45^\circ + 10j} = 2j A$$
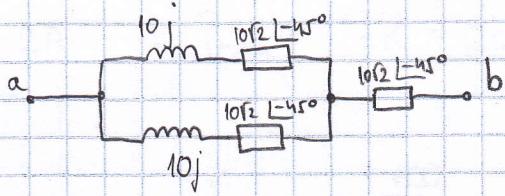
$$U_{ab} = -2j 10 \sqrt{2} \angle -45^\circ - 2j 10j + 10 \angle 90^\circ = -10j V$$



$$\dot{Z}_{ab} = 15 - j10 \quad //$$

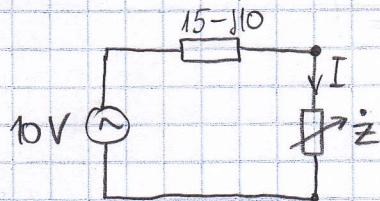

P_{MAX} :


$$R = |\dot{Z}_i|$$

$$\dot{Z} = \dot{Z}_i^* = 15 + j10$$

$$Z_{UK} = 30\Omega \rightarrow I = \frac{1}{3} A$$


$$P_{MAX} = I^2 \cdot R = \frac{1}{9} \cdot 15 = 5/3 W \quad //$$

Zad.)

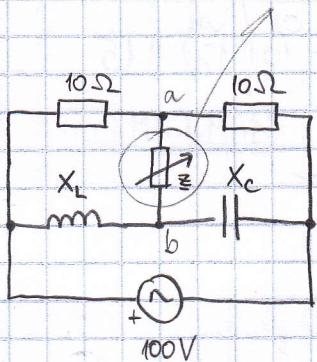


$I = 1A$ kroz \dot{Z} , bez obzira na njegov iznos
 $X_L, X_C = ?$

NORTON:

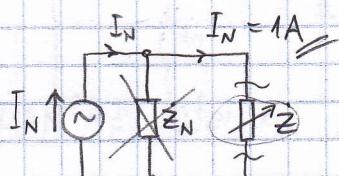


!! $\dot{z}_N \rightarrow \infty$ UVJEK U TAKVIM ZADACIMA !

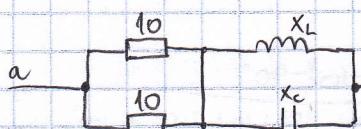↳ po Theveninu nema rješenja, pa moramo baš Norton!


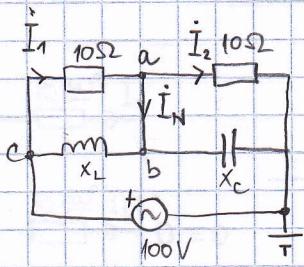
$$\begin{aligned} \dot{z}_N &= 10 \parallel 10 + (jX_L \parallel -jX_C) = \\ &= 5 + \frac{jX_L \cdot (-jX_C)}{(jX_L) - (-jX_C)} = 0 \rightarrow \text{da bi } \dot{z}_N \rightarrow \infty \\ &\downarrow \\ &X_L = X_C \end{aligned}$$



$$|I_N| = 1 \text{ A}$$

$$\dot{\varphi}_c = 100 \text{ V}$$

$$\dot{\varphi}_{a,b} \left(\frac{1}{10} + \frac{1}{jX_L} + \frac{1}{-jX_C} + \frac{1}{10} \right) - \dot{\varphi}_c \left(\frac{1}{10} + \frac{1}{jX_L} \right) = 0$$

nema izvora
izmene

$$\dot{I}_1 = \dot{I}_N + \dot{I}_2$$

$$\dot{I}_N = \dot{I}_1 - \dot{I}_2$$

$$\dot{I}_1 = \frac{\dot{\varphi}_c - \dot{\varphi}_a}{10} = 5 - \frac{50}{jX_L}$$


$$\dot{I}_2 = \frac{\dot{\varphi}_a}{10} = 5 + \frac{50}{jX_L}$$

$$\dot{I}_N = -\frac{100}{jX_L}$$

$$I = \sqrt{0^2 + \frac{100^2}{X_L^2}}$$




⋮



Zad 2.)

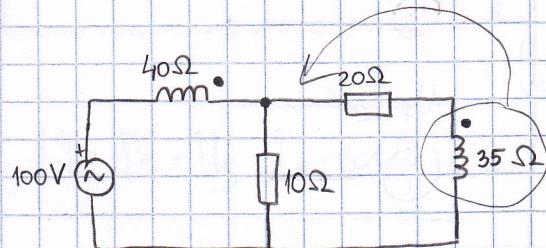

$$X_M = 15 \Omega$$

$$P_{MAX} = ?$$

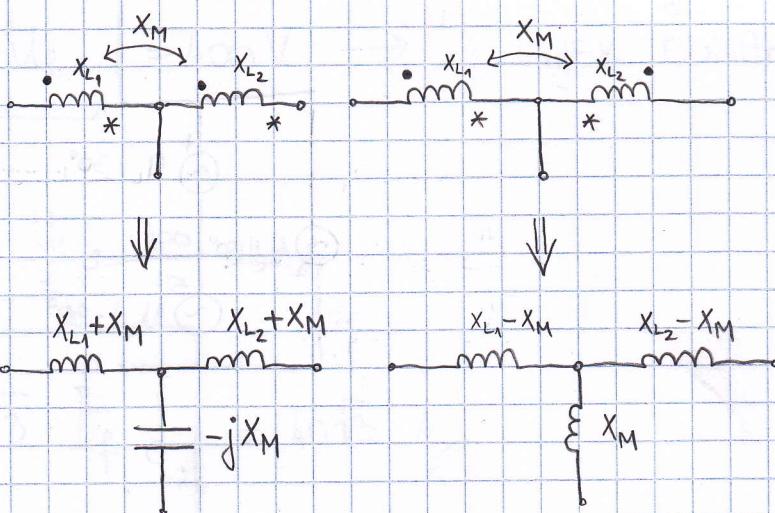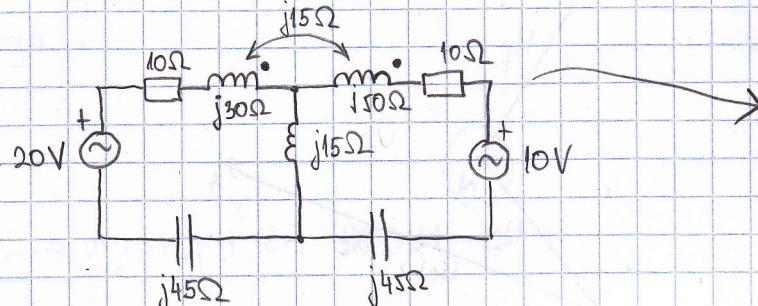
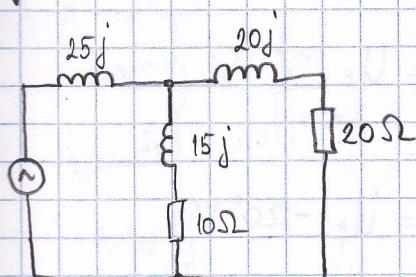


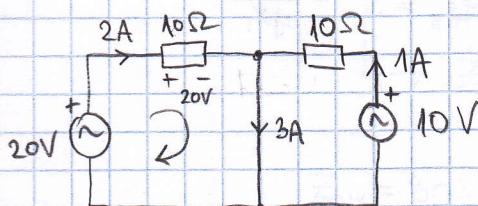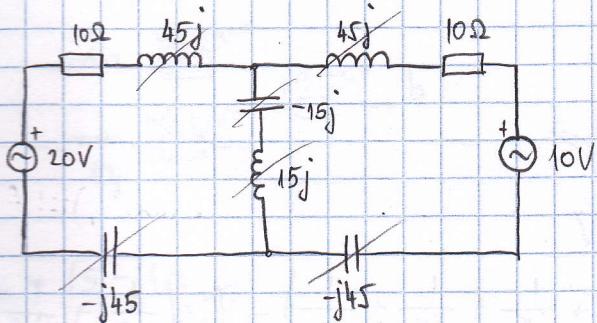

TROFAZNÍ:

$$\frac{U_f}{U_e} = \frac{230}{400}$$

$$U_f = \frac{U_e}{\sqrt{3}}$$

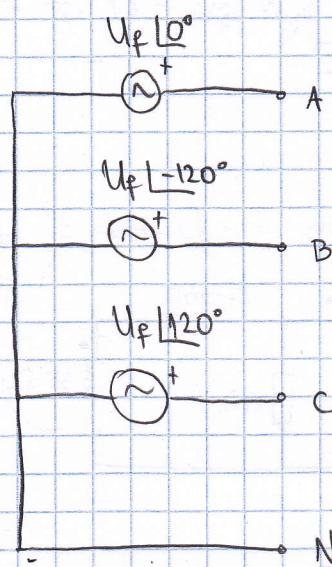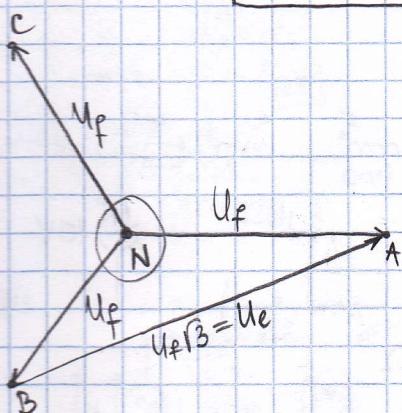


$$\dot{\varphi}_A = U_f | 0^\circ V$$

$$\dot{\varphi}_B = U_f | -120^\circ V$$

$$\dot{\varphi}_C = U_f | 120^\circ V$$

$$\dot{\varphi}_N = 0 V$$

SIMETRIČNO TROŠILO: ZVIJEZDA

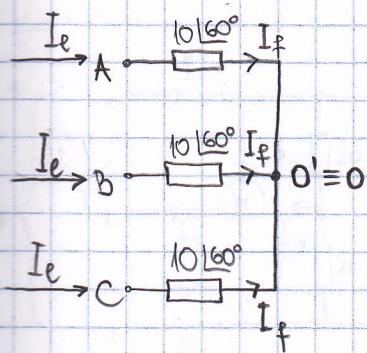

→ ako postoji NULNOD njegova je struja NULA!

$$I_o = 0 \text{ A}$$

$$U_f = \frac{U_e}{\sqrt{3}} \rightarrow \text{ZVIJEZDA}$$

$$I_f = I_e \rightarrow \text{I ZA NESIM}$$

$$U_f = 230 \text{ V}$$

bez kutova, svi su pomaknuti ...

$$I_f = \frac{230}{10} = 23 \text{ A}$$


$$P_{\Delta} = 3 \cdot U_f \cdot I_f \cdot \cos \varphi$$

} za OBA
SPOJA !

$$P = \sqrt{3} \cdot 400 \cdot 23 \cos 60^\circ \text{ (naš primjer)}$$

$$P_{\Delta} = \sqrt{3} \cdot U_e \cdot I_e \cdot \cos \varphi$$

TROKUT

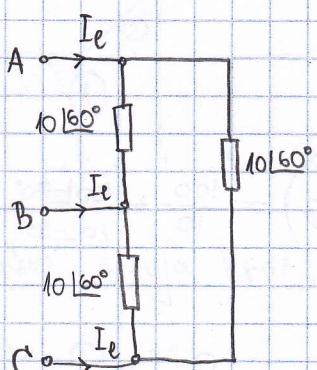

UVIJEK, I ZA NESIM

$$U_f = U_e$$

$$= 400 \text{ V} \rightarrow U_e \text{ UVIJEK JEDNAKI}$$


$$I_f = \frac{U_e}{Z} = \frac{400}{10} = 40 \text{ A}$$

$$I_e = \sqrt{3} \cdot I_f$$

$$= 40\sqrt{3} \text{ A}$$

$$P_{\Delta} = 3 P_{\lambda}$$

Zad.)

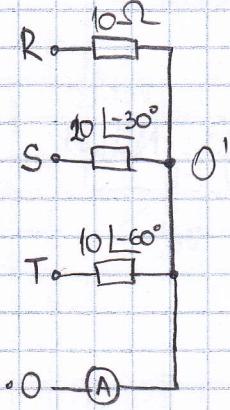

spojeno na $U_e = 73 \text{ V}$

$$\dot{\varphi}_{0'} = \dot{\varphi}_0 = 0 \text{ V} \rightarrow \text{zbog nulu voda}$$

$$\dot{\varphi}_R = 100 \text{ L } 0^\circ$$

$$\dot{\varphi}_S = 100 \text{ L } -120^\circ$$

$$\dot{\varphi}_T = 100 \text{ L } 120^\circ$$

$$\dot{I}_R = \frac{\dot{\varphi}_0 - \dot{\varphi}_{0'}}{10} = 10 \text{ A}$$

$$\dot{I}_S = \frac{\dot{\varphi}_S - \dot{\varphi}_{0'}}{20 \text{ L } -30^\circ} = 5 \text{ L } -90^\circ \text{ A}$$


$$\dot{I}_T = \frac{\dot{\varphi}_T - \dot{\varphi}_{0'}}{10 \text{ L } -60^\circ} = 10 \text{ L } 180^\circ = -10 \text{ A}$$

$$\dot{I}_0 = \dot{I}_R + \dot{I}_S + \dot{I}_T = 5 \text{ j}$$

$$I_A = 5 \text{ A}$$


→ umjesto ---A--- dosao ---V---

→ moramo naci $\dot{\varphi}_0$

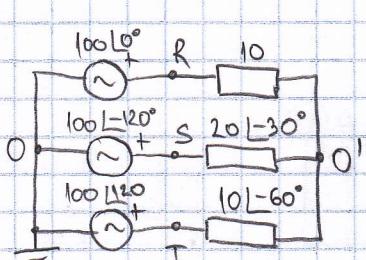

$$\dot{\varphi}_0 \left(\frac{1}{10} + \frac{1}{20 \text{ L } -30^\circ} + \frac{1}{10 \text{ L } -60^\circ} \right) = \frac{100}{10} + \frac{100 \text{ L } -120^\circ}{20 \text{ L } -30^\circ} + \frac{100 \text{ L } -60^\circ}{10 \text{ L } -60^\circ}$$

NESIMETRIČNO, TROKUT:

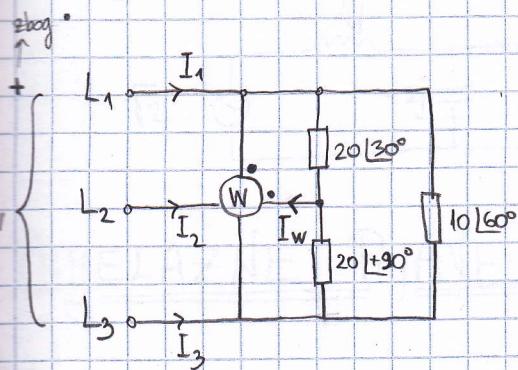

izvor $U_e = 400 \text{ V}$

$$\dot{\varphi}_1 = 230 \angle 0^\circ$$

$$\dot{\varphi}_2 = 230 \angle -120^\circ$$

$$\dot{\varphi}_3 = 230 \angle 120^\circ$$

$$\dot{U}_w = \dot{U}_{13} = \dot{\varphi}_1 - \dot{\varphi}_3 = 400 \angle -30^\circ$$



$$P_w = \operatorname{Re} \{ \dot{U}_w \cdot \dot{I}_w^* \} = U \cdot I \cdot \cos(\delta_u - \delta_i)$$

$$\dot{I}_w = \dot{I}_{12} + \dot{I}_{32} = \frac{\dot{\varphi}_1 - \dot{\varphi}_2}{20 \angle 30^\circ} + \frac{\dot{\varphi}_3 - \dot{\varphi}_2}{20 \angle +90^\circ} = 20 + 20 = 40 \text{ A}$$

$$P_w = 400 \cdot 40 \cos(-30^\circ - 0^\circ)$$

NESINUSNI VALNI OBLICI:


1)

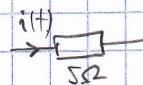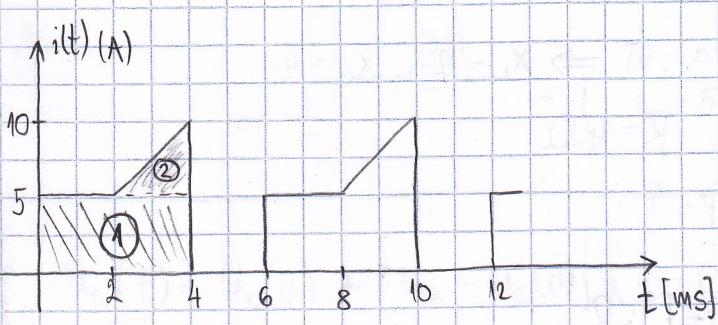

→ takva struja kroz otpor $R=5 \Omega$, $P_{SR} = ?$

$$P_{SR} = P = I^2 \cdot R$$


$$T = 6 \text{ ms}$$

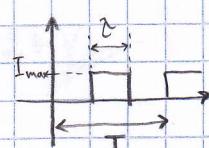

$$I_{SR} = I_m \cdot \frac{T}{T}$$

$$I_{SR} = \frac{1}{T} \int_T i(t) dt$$

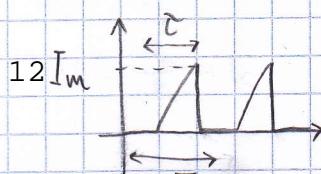
$$I_{EF} = \sqrt{\frac{1}{T} \int_T i^2(t) dt}$$



$$I_{EF} = I_m \cdot \sqrt{\frac{2}{T}}$$

$$I_{SR} = \frac{I_m}{2} \cdot \frac{T}{T}$$
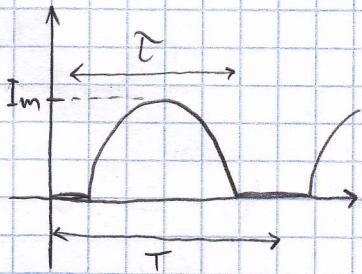
$$I_{EF} = \frac{I_m}{\sqrt{3}} \cdot \sqrt{\frac{2}{T}}$$



$$I_{SR} = \frac{I_m}{\pi} \cdot \frac{\pi}{T}$$

$$I_{ef} = \frac{I_m}{T/2} \cdot \sqrt{\frac{\pi}{T}}$$

$$I_{EF} = \sqrt{I_{EF_1}^2 + I_{EF_2}^2 + \dots}$$

$$I_{SR} = I_{1SR} + I_{2SR}$$

①

$$\left. \begin{array}{l} I_{1m} = 5 \\ \tau_1 = 4 \text{ ms} \end{array} \right\} I_{ef_1} = 5 \cdot \sqrt{\frac{4}{6}}$$

②

$$\left. \begin{array}{l} I_{2m} = 5 \\ \tau_2 = 2 \text{ ms} \end{array} \right\} I_{ef_2} = \frac{5}{\sqrt{3}} \cdot \sqrt{\frac{2}{6}}$$


preko integrala:

$$I_{ef} = \sqrt{\frac{1}{6 \text{ ms}}} \left[\int_{0 \text{ ms}}^{2 \text{ ms}} 5^2 dt + \int_{2 \text{ ms}}^{4 \text{ ms}} \left(\frac{5}{2}t\right)^2 dt + \int_{4 \text{ ms}}^{6 \text{ ms}} 0^2 dt \right]$$

$y - 5 = \frac{5}{2}(t - 2)$
 $y = \frac{5}{2}t$

Pr. 2)
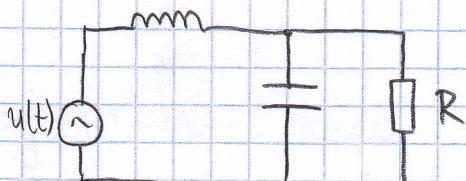
$$u(t) = 4 + 10 \sin(\omega t) + 2 \sin(2\omega t) = u_1 + u_2 + u_3$$



$$\text{na } \omega \Rightarrow X_L = 2, X_C = 4$$


$$R = 4 \Omega$$

$$P = ?$$


$$P = I^2 \cdot R$$

$$u_2 = 10 \sin(\omega t) \rightarrow U_2 = \frac{10}{j\omega} = U_{2ef}$$
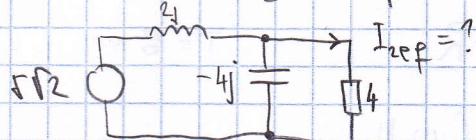
$$\frac{1}{j\omega} \quad I_1 = I_{SR} = I_{ef} = 1A$$







$$U_3 = \frac{2}{R_2} = U_{3\text{ef}}$$

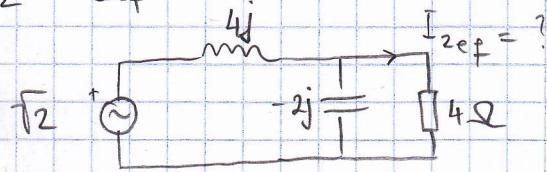

PRIJELAZNE PoJAVE:


Zad.)

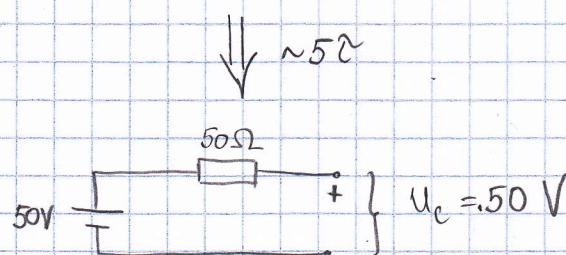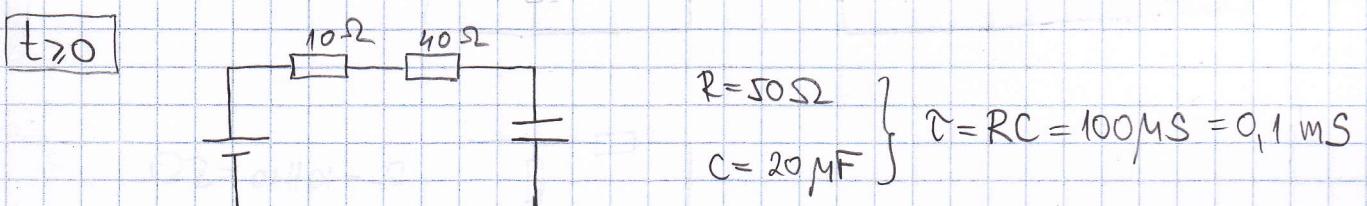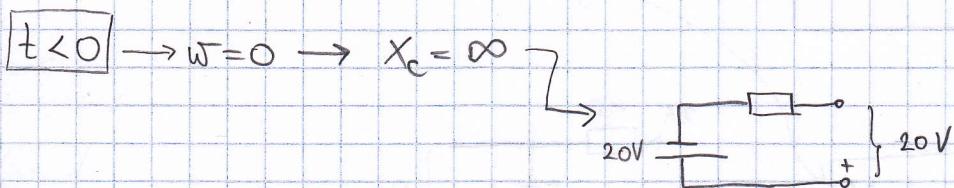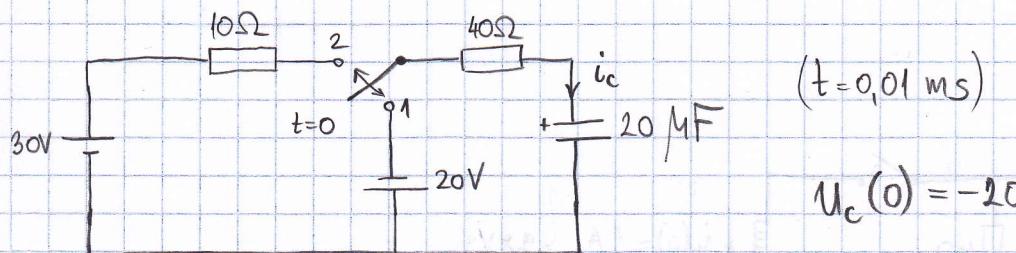

$$U_c(t) = U_c(0) + [U_k - U_c(0)] \left(1 - e^{-\frac{t}{\tau}}\right)$$

$$U_c(t) = -20 + 70 \left(1 - e^{-1}\right)$$
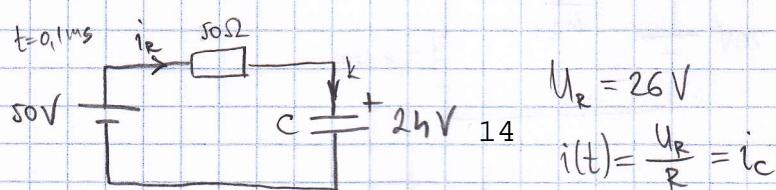
$$U_c(t=0,1 \text{ ms}) = -20 + 70 \left(1 - e^{-1}\right) = 24 \text{ V}$$




RL:

$$C = \frac{L}{R}$$



$$u(t) = u(0) + [I_k - i_k(0)] (e^{-\frac{t}{C}})$$

Zad.)

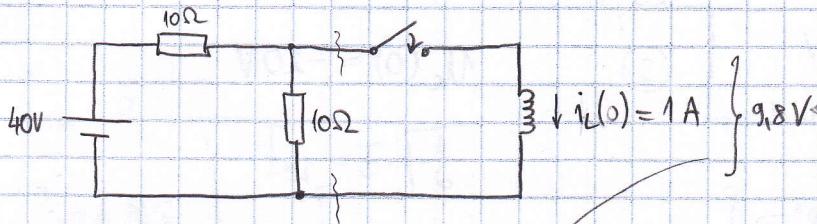

$$L = 50 \text{ mH}$$

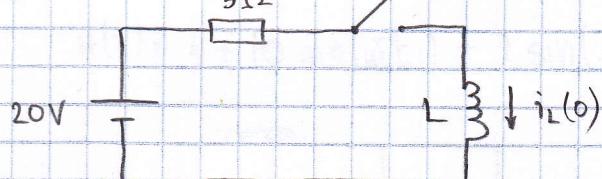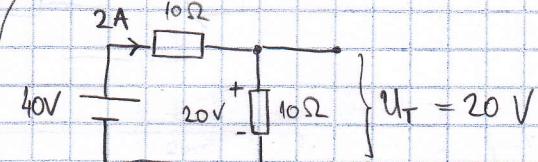
$$U_{R_2}(t=0,01 \text{ s}) = 9,8 \text{ V}$$



$$R_T = 10 \parallel 10 = 5\Omega$$

$$C = \frac{L}{R}$$

nakon $> 5\Omega$

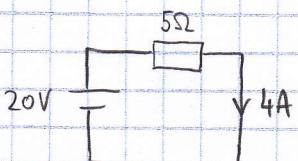

$$u(t) = 1 + 3 e^{-\frac{t}{C}}$$

$$u(0,01 \text{ ms}) = 1 + 3e^{-1} = 2,1 \text{ A}$$

